



# CMPT 295

Unit – Microprocessor Design & Instruction Execution

Lecture 27 – Combinational and Sequential Logic Circuits

# Last Lecture

- We have now started to explore how the microprocessor executes machine instructions (series of 0's and 1's)
  - More specifically, how its **datapath** can be constructed
- **Microprocessor** itself is ...
  - Made of resistors, capacitors, diodes, and transistors
  - Billions of them, so understanding how these small components work together is too detailed hence too onerous
  - So we resort to abstraction (**black box**) in order to understand their functioning
    - We use **logic gates** to abstract the “how these small components work together” by highlighting “what they do”, i.e., **perform a Boolean function**
  - What is important for us to understand is that hardware components (such as logic gates) have **propagation delay**
    - Signals (0's and 1's) take time to propagate through them

# Today's Menu

- Instruction Set Architecture (ISA)
  - Definition of ISA
- Instruction Set design
  - Design principles
  - Look at an example of an instruction set: MIPS
  - Create our own
  - ISA evaluation
- Implementation of a microprocessor (CPU) based on an ISA
  - Execution of machine instructions (datapath)
  - Intro to logic design + Combinational logic + Sequential logic circuit
  - Sequential execution of machine instructions
  - Pipelined execution of machine instructions + Hazards

# From our last lecture - Digital circuits

- In order to understand **how the microprocessor executes these machine instructions (series of 0's and 1's)**, we need to have a look at the components of a microprocessor and how they function:

1. Combinational logic -> manipulate bits (compute functions on bits e.g., ADD)
2. Memory elements -> store bits
3. Clock signals -> regulate the update of memory elements

and what affects the execution speed of these components such as **propagation delay**



- So, we need to understand a few things about **digital circuits**

Types of components  
found in a digital system  
such as a  
microprocessor

- output depends only on input
- given same input produces same output
- no internal storage
  
# Combinational logic circuits - 1

- Made by connecting several logic gates together
- Compute more complex functions than just AND or XOR
- **Example:** Combinational logic circuit that adds 2 bits together



- Propagation delay: "1 gate" delay
- <http://sullystationtechnologies.com/ichalfadder.html>


# Example of an integrated circuit (IC)

## SN74LVC2G157


 
### 2G157

SINGLE 2-LINE TO 1-LINE DATA  
SELECTOR/MULTIPLEXER




# More examples in our Textbook

- Combinational circuit to test for bit equality -> Figure 4.10
- Combinational circuit to test for word equality -> Figure 4.12
- Single-bit multiplexor circuit -> Figure 4.11
- Word-level multiplexor circuit -> Figure 4.13
 
# Combinational logic circuits - 2

- Can connect several combinational logic circuits together to perform more complex functions and/or to perform function on a wider input
- What does this circuit do?



- Propagation delay: "3 gate" delay




# Hw: Label all input & output lines!
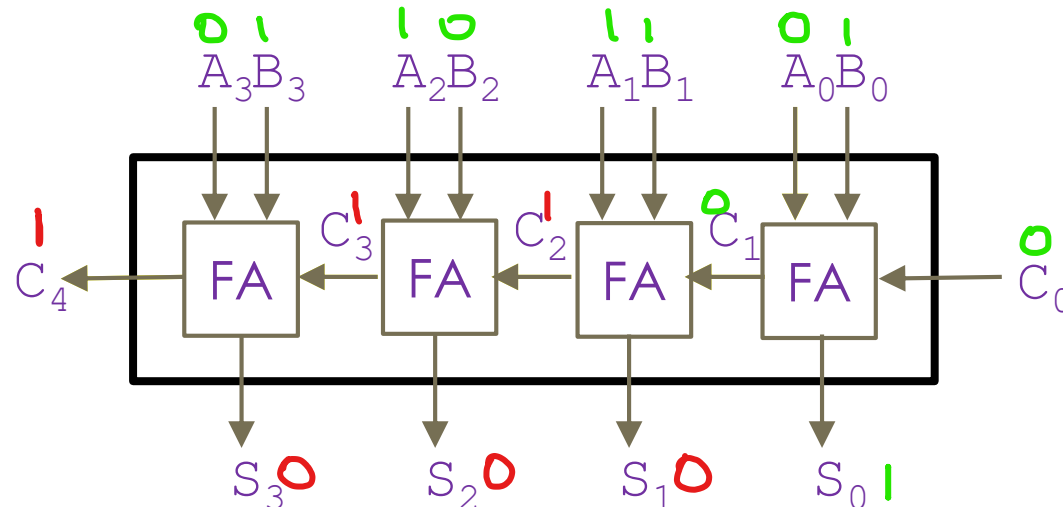
## Combinational logic circuits - 3


- Can connect several combinational logic circuits together as **black boxes** (black box design can be modular)
- The resulting circuit can operate on word size data such as integral values and memory addresses
- Example:** Full Adder operating on data of word size 4 ( $w = 4$ )  
aka 4-bit ripple carry adder

$C_3 \ C_2 \ C_1 \ C_0$   
1 1 0 0  
A 0 1 1 0  
+ B 1 0 1 1  
-----  
S<sub>3</sub> S<sub>2</sub> S<sub>1</sub> S<sub>0</sub>  
0 0 0 1  
C<sub>4</sub>




- Propagation delay?

 Block Diagram  
of Full Adder ( $w = 4$ )



where ...

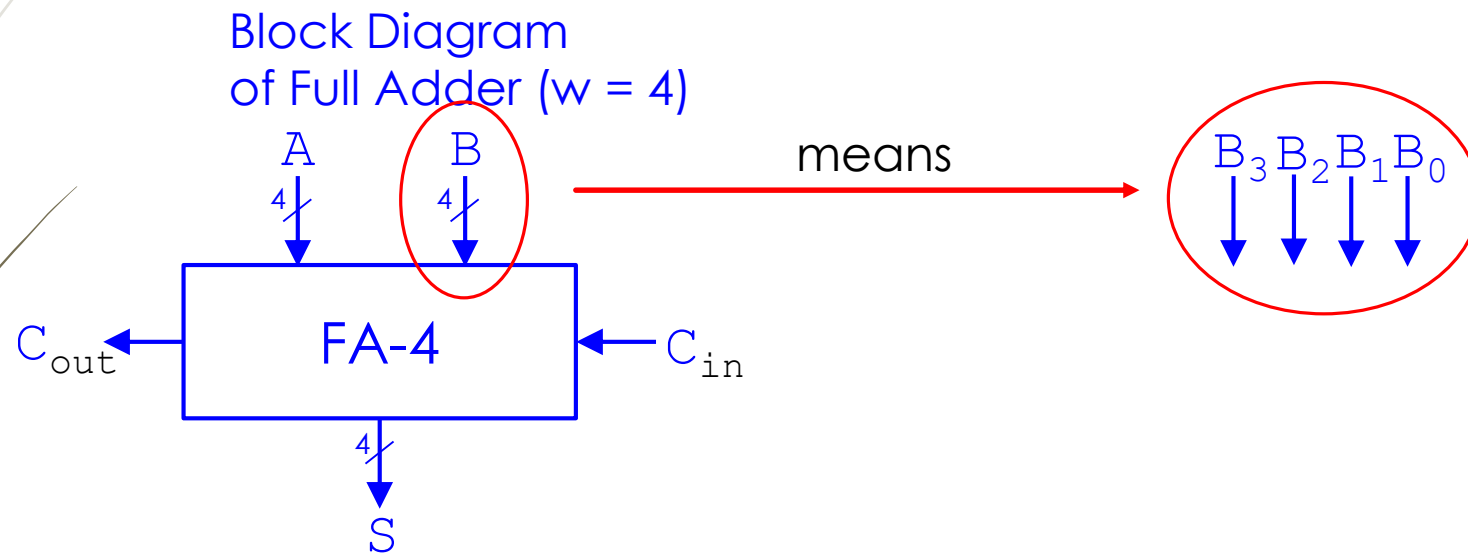

Why is the propagation delay of this Full Adder 4 (also known as a 4-bit (w-bit) ripple carry adder) 9 gates ( $2w + 1$  gates) where  $w$  is the number of bits (as opposed to 12 gates  $\rightarrow 4 \times 3$  p.d.)?

↑ gate




Bit 1

Bit 2

Bit 3
 
# ALU - Example of combinational logic circuit


- Arithmetic/logic unit found in microprocessor
  - Black box diagram
- ALU executes *data manipulation machine instructions* (defined in the ISA)



S	operation
0001	A + B
0010	A - B
1000	A * B
0100	A ^ B
0101	A & B
 
# Summary: Combinational logic circuits

- **Definition:** A combinational logic circuit computes a function, where its outputs is based only on its inputs
- Contains logic gates
  - Input values propagate through logic gates of combinational logic circuit whenever they change
  - Input to a logic gate must come from either input of combinational logic circuit itself (input to black box) or output of other logic gates
  - Outputs of two or more logic gates cannot be connected together unless it is via a logic gate
- Acyclic: there are no feedback loops
- Does not require a clock signal, does not contain memory elements -> does not store (remember) anything



# From our last lecture - Digital circuits

- In order to understand **how the microprocessor executes these machine instructions (series of 0's and 1's)**, we need to have a look at the components of a microprocessor and how they function:

Types of components  
found in a digital system  
such as a  
microprocessor

1. Combinational logic -> manipulate bits (compute functions on bits e.g., ADD)

2. Memory elements -> store bits

**Sequential  
logic circuit**


3. Clock signals -> regulate the update of memory elements

and what affects the execution speed of these components such as **propagation delay**

- So, we need to understand a few things about **digital circuits**

 
# Sequential logic circuit


- Has a state -> memory (it has internal storage)
- “Clocked”
  - Has at least 2 input:
    - Data to be remembered and
    - Clock
  - Has at least one output:
    - Value remembered (during an earlier clock cycle)
- Example of a sequential logic circuit is a memory element
- Simplest memory element: D-type flip-flop
- Example of memory element components with which we are already familiar: registers



**1G79**  
SINGLE POSITIVE-EDGE-TRIGGERED  
D-TYPE FLIP-FLOP
 
# Memory elements and Clock signals

- Memory element #1 -> **clocked registers a.k.a. hardware registers**
  - On the microprocessor
  - A clocked register stores 1 bit (state)
  - Synchronized by system-wide clock
- System-wide clock
  - A system-wide clock sends 0 1 0 1 0 1 0 1...
  - **Clock period**: 1 full cycle duration: 
  - **Clock frequency**:  $1/\text{period}$
- How **clocked registers** work:
  - Output current state
  - Input next state
  - Next state remembered only on **rising edge of clock**






## Function Table


Load	D	$Q(t + 1) \rightarrow$ next state
0	X	$Q(t) \rightarrow$ current state
1	0	0
1	1	1

## How a *clocked register* function!

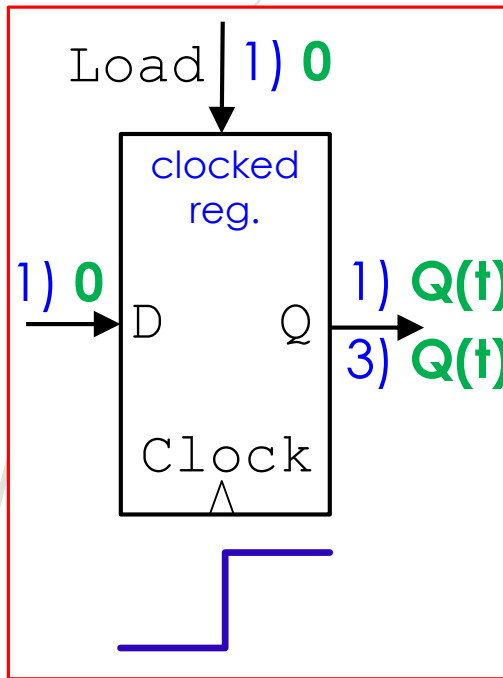


2) When the clock "ticks", i.e., when edge of clock rises

Row 1 of Function Table

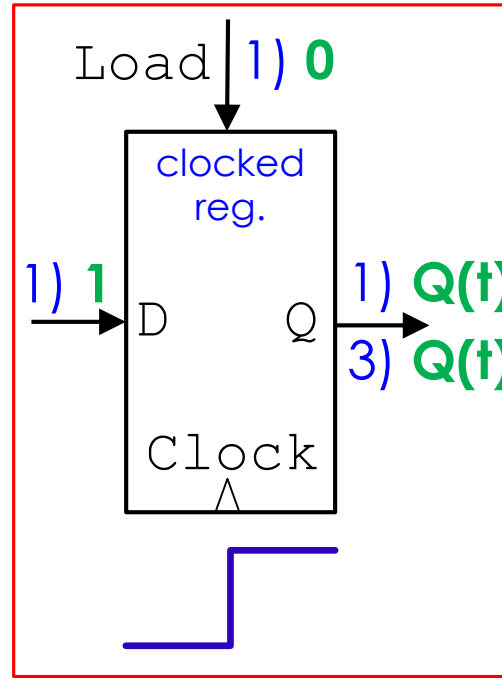


2) When the clock "ticks", i.e., when edge of clock rises

Row 1 of Function Table

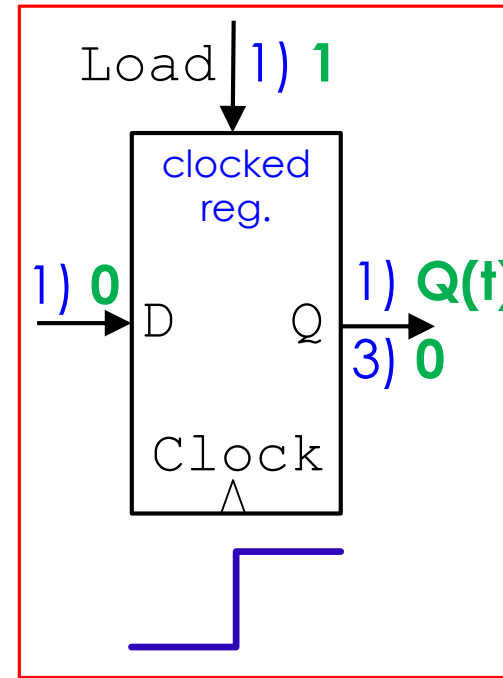

2) When the clock "ticks", i.e., when edge of clock rises

Row 2 of Function Table

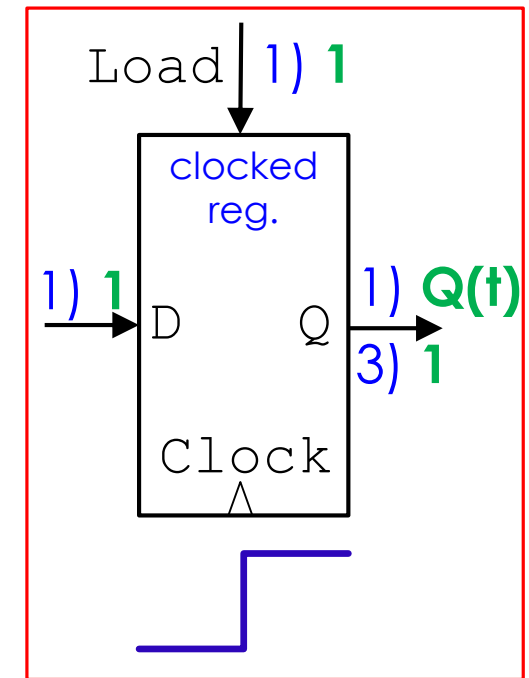


2) When the clock "ticks", i.e., when edge of clock rises


Row 3 of Function Table

# Timing Diagram

Edge-triggered clock

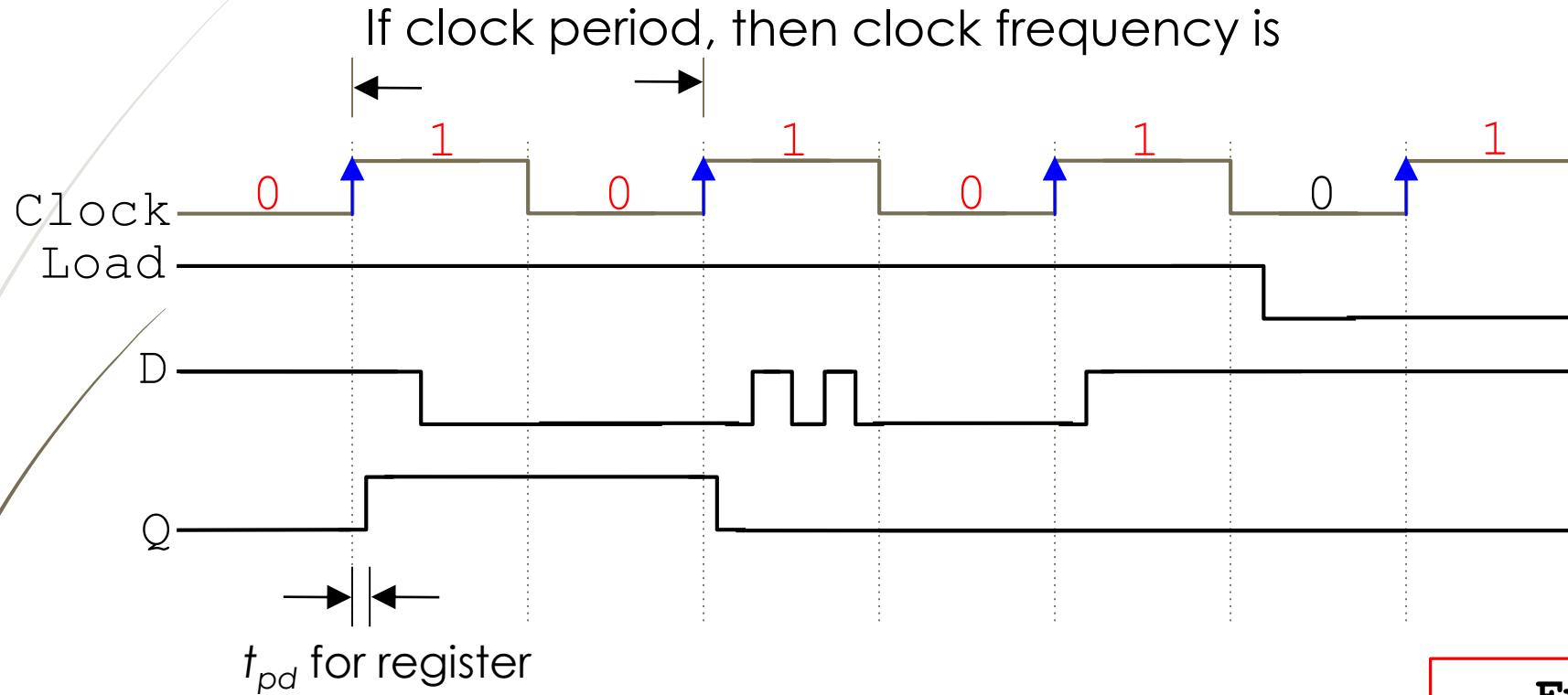

D flip flop

 

Function Table

Load	D	$Q(t + 1)$
0	X	$Q(t)$
1	0	0
1	1	1

# Summary

- ✓ Combinational logic circuits
  - Made of many logic gates
  - Multi-functional combinational logic circuits such as ALU have control input lines to indicate which function to perform
  - Combinational logic circuits do not store (remember) values
- ✓ Sequential logic circuits
  - Made of combinational logic circuits, memory elements (clocked registers) and clock
  - Circuit that “remembers” values (state) and perform computations on these values

# Next Lecture

- Instruction Set Architecture (ISA)
  - Definition of ISA
- Instruction Set design
  - Design principles
  - Look at an example of an instruction set: MIPS
  - Create our own
  - ISA evaluation
- Implementation of a microprocessor (CPU) based on an ISA
  - Execution of machine instructions (datapath)
  - Intro to logic design + Combinational logic + Sequential logic circuit
  - Sequential execution of machine instructions
  - Pipelined execution of machine instructions + Hazards